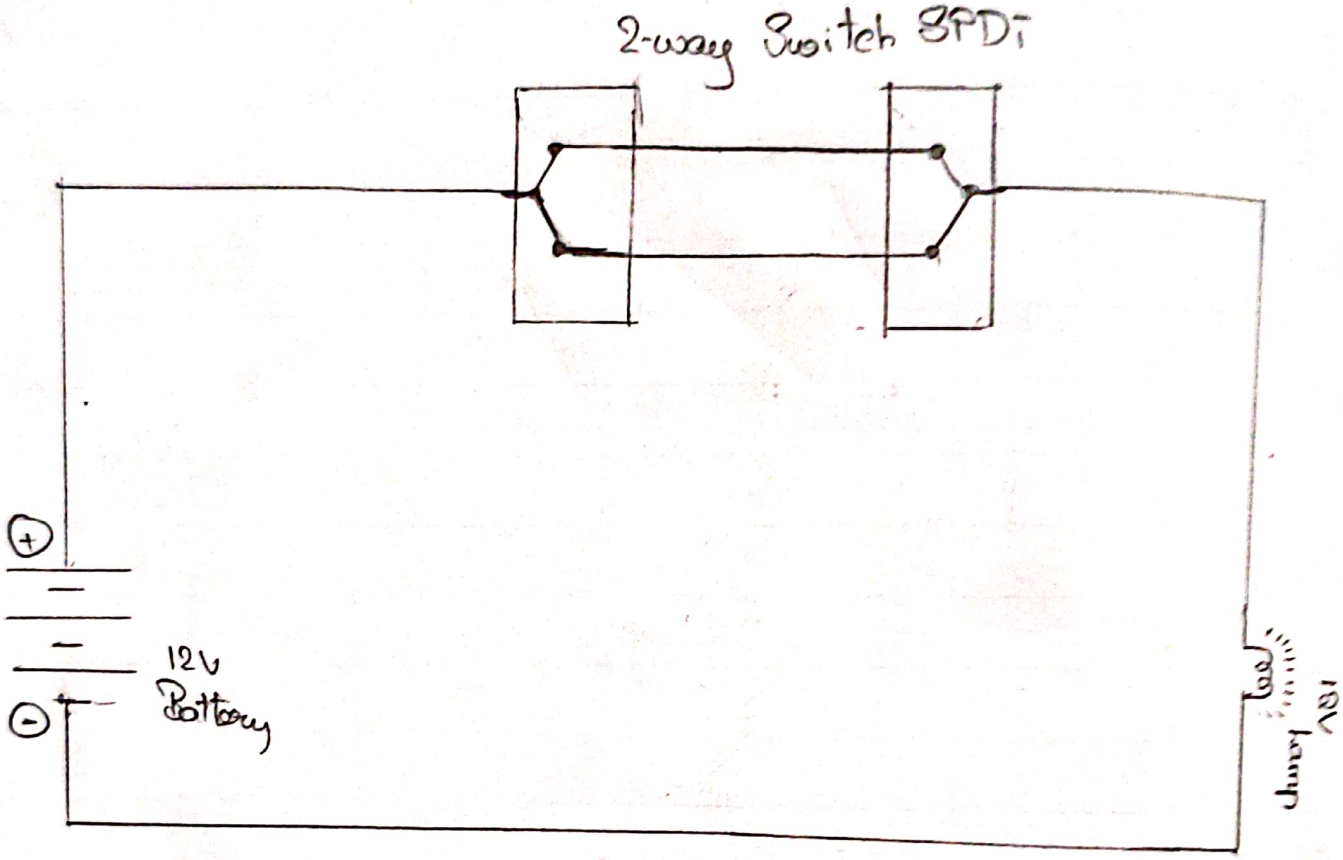

SPDT - SINGLE POLE DOUBLE THROW SWITCH

Scanned with OKEN Scanner

Staircase Wiring

AIM:-

To develop and test the staircase wiring using proteus.

Apparatus Required:-

Laptop with proteus software.

Theory:-

Staircase wiring is a common multiple way switching or two way switching connection. It involves wiring for one light with two switches. In this set up is controlled by two switches located operate the load from separate position above or below the staircase from inside or outside of room or two way lod switch.

PROCEDURE:-

* Drag the required components from the process library.
* Connect the components as per circuit diagram.
* Run the simulation and check the lamp for different switching condition.

SAVEETHA ENGINEERING COLLEGE SAVEETHA NAGAR 602 105 BE THE BEST

Scanned with OKEN Scanner

GRASS CONNECTION

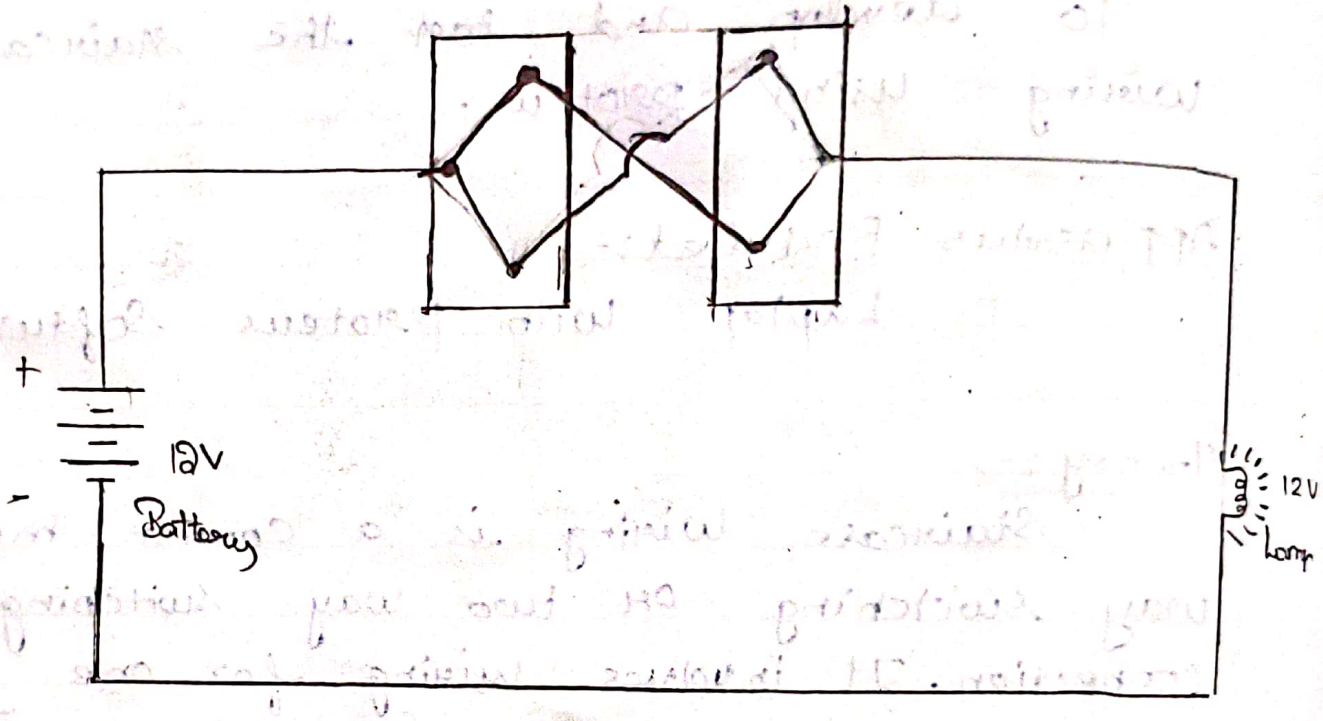

Scanned with OKEN Scanner

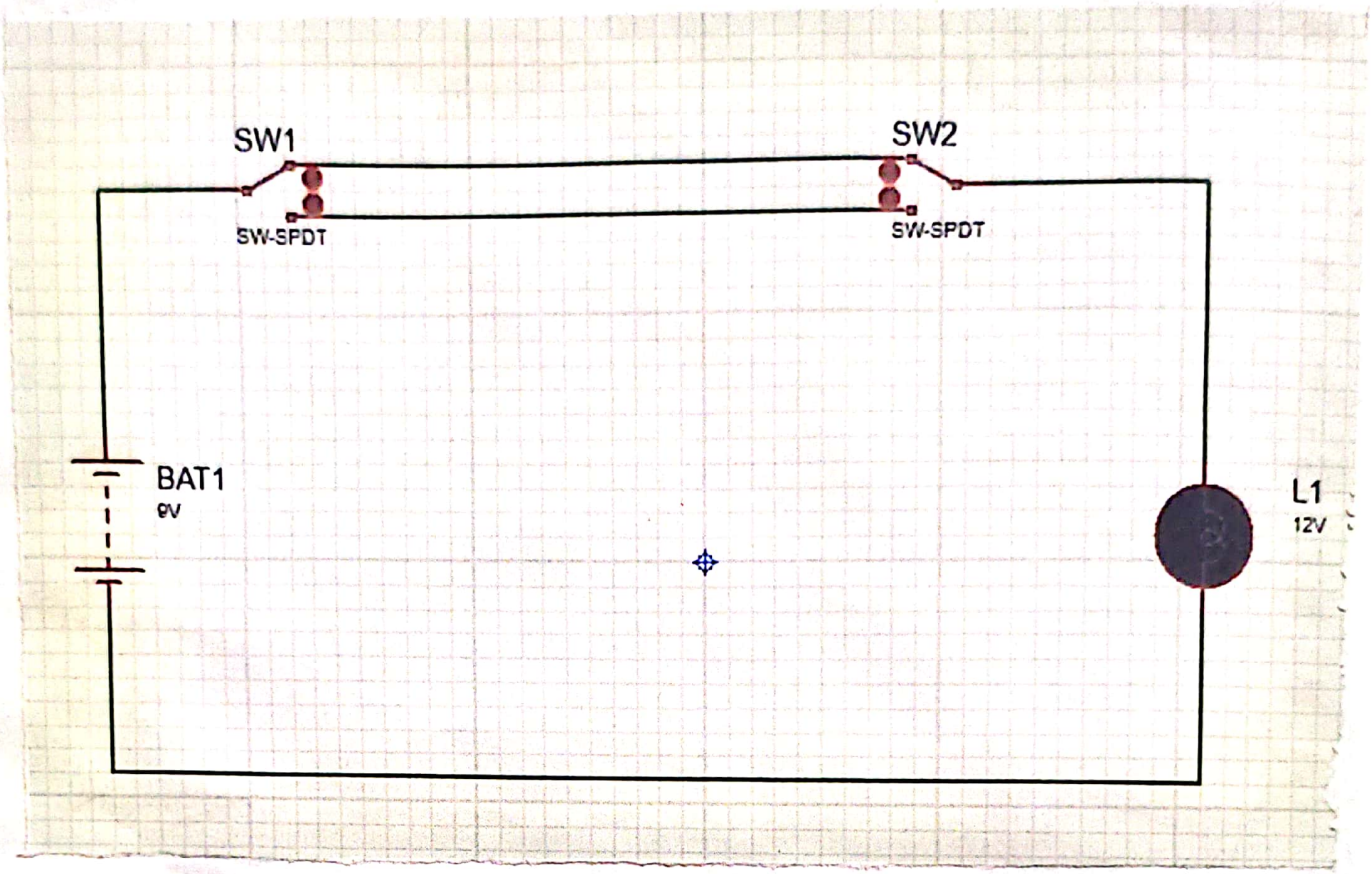

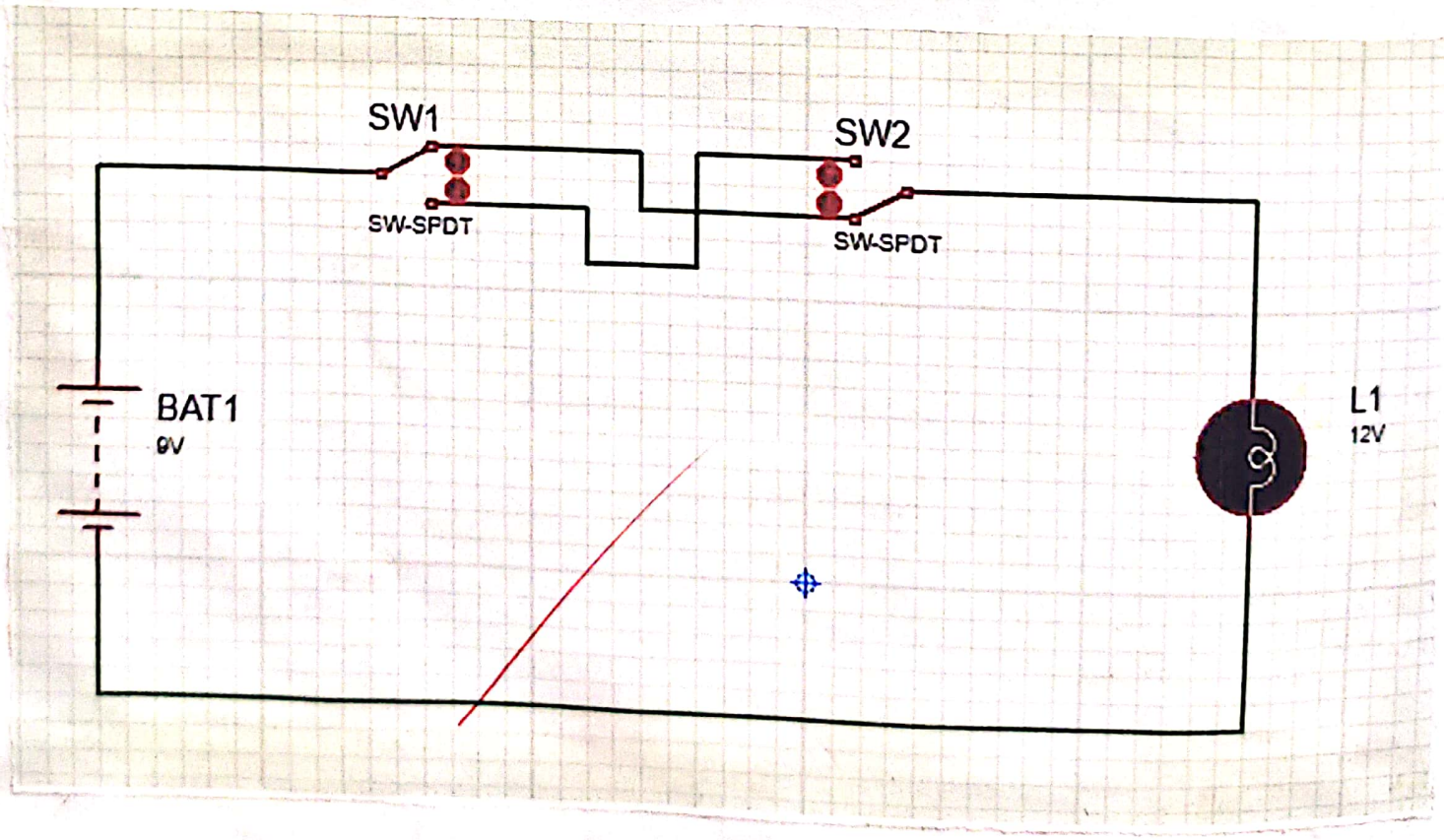

Scanned with OKEN Scanner

Expt. No.

SAVEETHA
ENGINEERING COLLEGE
SAVEETHA NAGAR 602 105
BE THE BEST

99

18/03/26

RESULT :-

Thus the staircase using connection wire developed and tested successfully.

Scanned with OKEN Scanner